

EE 315 Course Project:

General Description & Individual Preparation


2/27/2023

EE 315, V. Prodanov

1

1

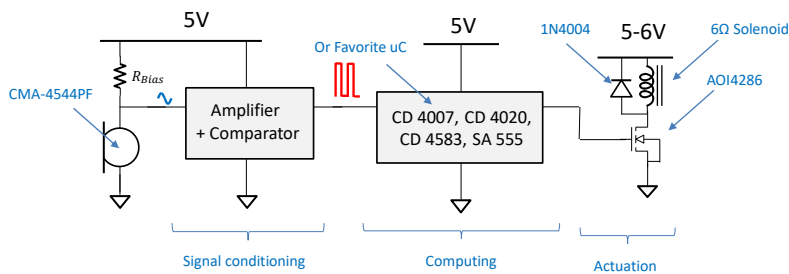EE 315 Course Project: General Description



Desired Functionality:

- The solenoid is energized when the frequency of the audio tone > target frequency (no response if the frequency is < target) *You decide the value*
- (much) Harder: Actuate within a narrow frequency range only *Required if you use a Micro-Controller*

2/27/2023

EE 315, V. Prodanov


2

2

Individual Preparation: 15% of Course Grade

Design and Verify in Spice:

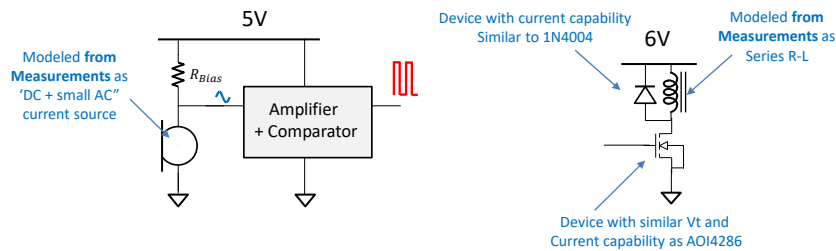- The Front-End Circuitry (Amp + Comparator)
- The FET-Solenoid Actuator




2/27/2023

EE 315, V. Prodanov

3

3

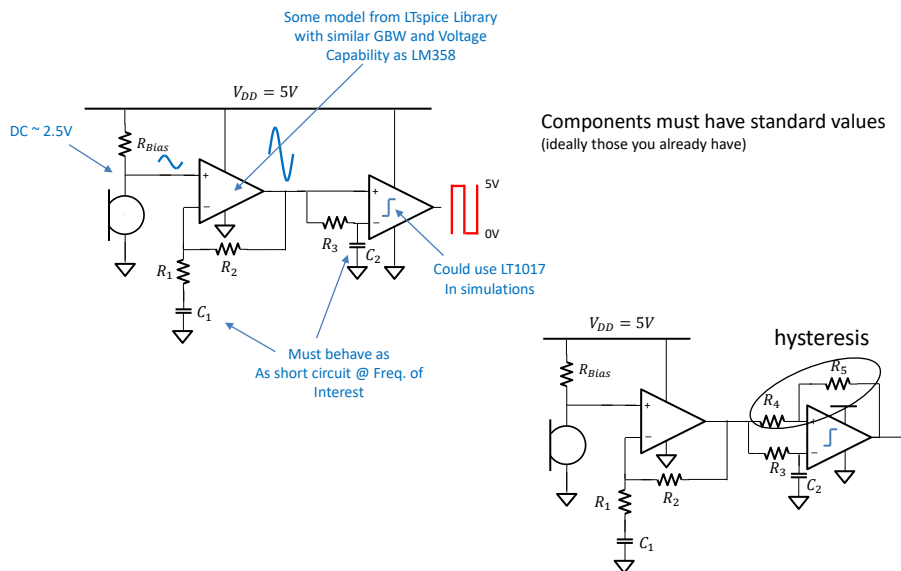Amplifier + Comparator Architectures: Select One




2/27/2023

EE 315, V. Prodanov

4

4

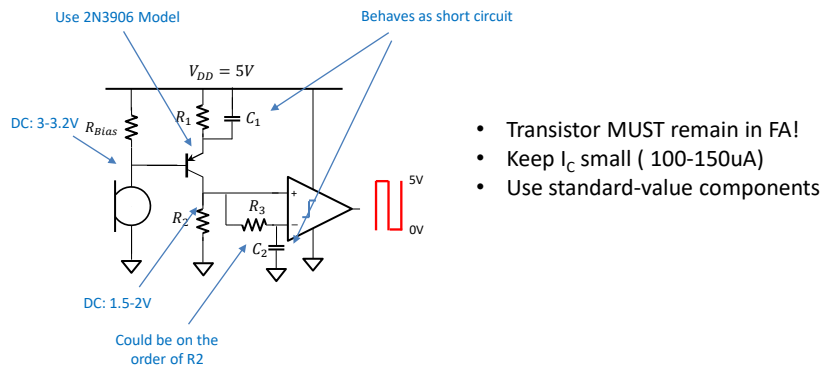Alternative Amplifier + Comparator Architectures



Hysteresis can be created by connecting single Resistor between the output of the comparator and comparator “+” node.

2/27/2023

EE 315, V. Prodanov

5

5

Provide a PPT containing the following

1. SPICE print-out of Schematics (must contain component values)
2. AC simulation results of amplifier (outputs taken at R_2 and C_3)
 - Log frequency 10Hz to 100kHz
3. Transient Response of amplifier + comparator (output taken at R_2 and Comparator output)
 - Input signal: AC current with magnitude of 1uA @ the chosen frequency
4. FET Solenoid Driver & Diode (output taken at the drain of the FET)
 - Input signal: 0-5V square-wave
5. A paragraph explaining how the team plans to implement the ‘decision-making’ digital circuit

This ASSIGNMENT is INDIVIDUAL. PLEASE Complete ALONE.

2/27/2023

EE 315, V. Prodanov

6

6